

PE STRING ENSEMBLE

A.J. BOOTHMAN B.Sc.

Part 4

THE Voice circuitry of the String Ensemble is primarily designed to produce a basic tone which when processed through the Chorus Generator gives the simulated sound of an orchestral string section. Two other voices are also provided to add variety to the overall effect and have the basic characteristics of Woodwind and Brass instruments. The circuitry includes the facility to vary the degree of mixing of the voices, and the switching which enables changes of register to be made in both upper and lower sections of the keyboard.

THE VOICING SYSTEM

The outline of the voicing system is shown in Fig. 4.1, and consists of two sections covering upper and lower parts of the keyboard separately. Outputs from the threshold diodes, following the diode gates, for the upper section of the keyboard are taken to staircase networks in the voicing system

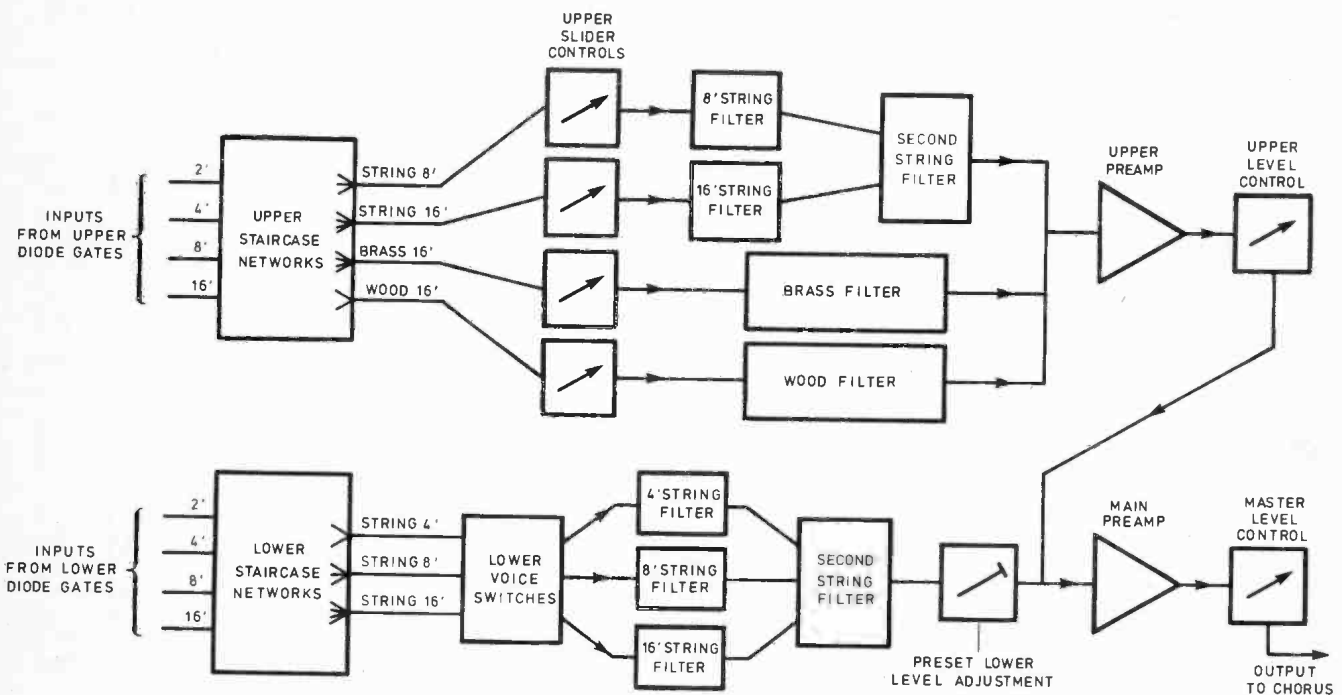


Fig. 4.1. Schematic of the voicing system

which produce stepped waveforms suitable for the four instruments, three at 16ft pitch and one at 8ft pitch. Each instrument is controlled by a slider potentiometer and has its own filter. The string voicing consists of a combination of both high and low pass filters which in conjunction with the second filter, which processes both registers, are in active form. Brass and Woodwind voices are produced by ringing band pass active filters and following a common preamplifier all upper voices are adjusted by a level control on the front panel.

A similar staircase network section produces stepped waveforms for strings in the lower section of the keyboard at 16ft, 8ft, and 4ft, which are then controlled by the lower voice switches and followed by similar string filters to the upper section with a preset level control on the Voice Board.

The combined voices from the full keyboard are amplified together and set by the master level control on the front panel. This signal is passed to the Chorus Generator for processing and returned to the Voice Board for distribution to the Swell Pedal and output sockets.

STAIRCASE NETWORKS

The effect of the Staircase networks is shown in Fig. 4.2 where waveforms (a) to (d) are square waves at 2ft, 4ft, 8ft, and 16ft each coming from the respective diode gate busbar. The square waves contain odd harmonics only which have limited use in the generation of musical instrument tones. Since the square waves on each busbar are octave related even harmonics are available by mixing outputs from each busbar. Generally an amplitude relationship is used where the level of each successively higher even harmonic content is half that of the harmonic below.

Waveform (e) in Fig. 4.2 is produced by mixing an input at 16ft (d) with half the level at 8ft (c), and is used as the base waveform for the woodwind. The description "staircase" can be understood from the shape obtained. Waveform (f) is produced by mixing an input at 16ft with half the level at 8ft, a quarter the level at 4ft, and one eighth the level at 2ft. This waveform is used for all 16ft strings and brass, giving the addition of higher even harmonics.

Waveform (g) is obtained by mixing a fundamental at 8ft with half the level at 4ft and a quarter the level at 2ft for the 8ft strings, whilst waveform (h) has a fundamental at 4ft with half the level at 2ft and is used for the 4ft strings in the lower section.

VOICE CIRCUITRY

Full circuit details are given in Fig. 4.3. Resistors R69 to R76 terminate the output busbars from the diode gate circuits and are essential in any tests of the diode gate system if the Voice Board is removed. R77 to R98 perform the staircasing function prior to slider or switch controllers. The upper string filters are associated with IC32, the brass with IC33, woodwind with IC34 and lower strings with IC35. VR16 and VR17 control the resonant frequencies of the brass and woodwind filters respectively and require setting to avoid the violent peak occurring within the keyboard range. IC36 amplifies all the upper voices and is followed by the upper level control VR18.

LOWER STRING CONTROLS

Switches S3 to S6 are interlinked. With S3 depressed the 16ft and 8ft waveforms from the lower section of the keyboard are linked to String I and II slider controls respectively, and

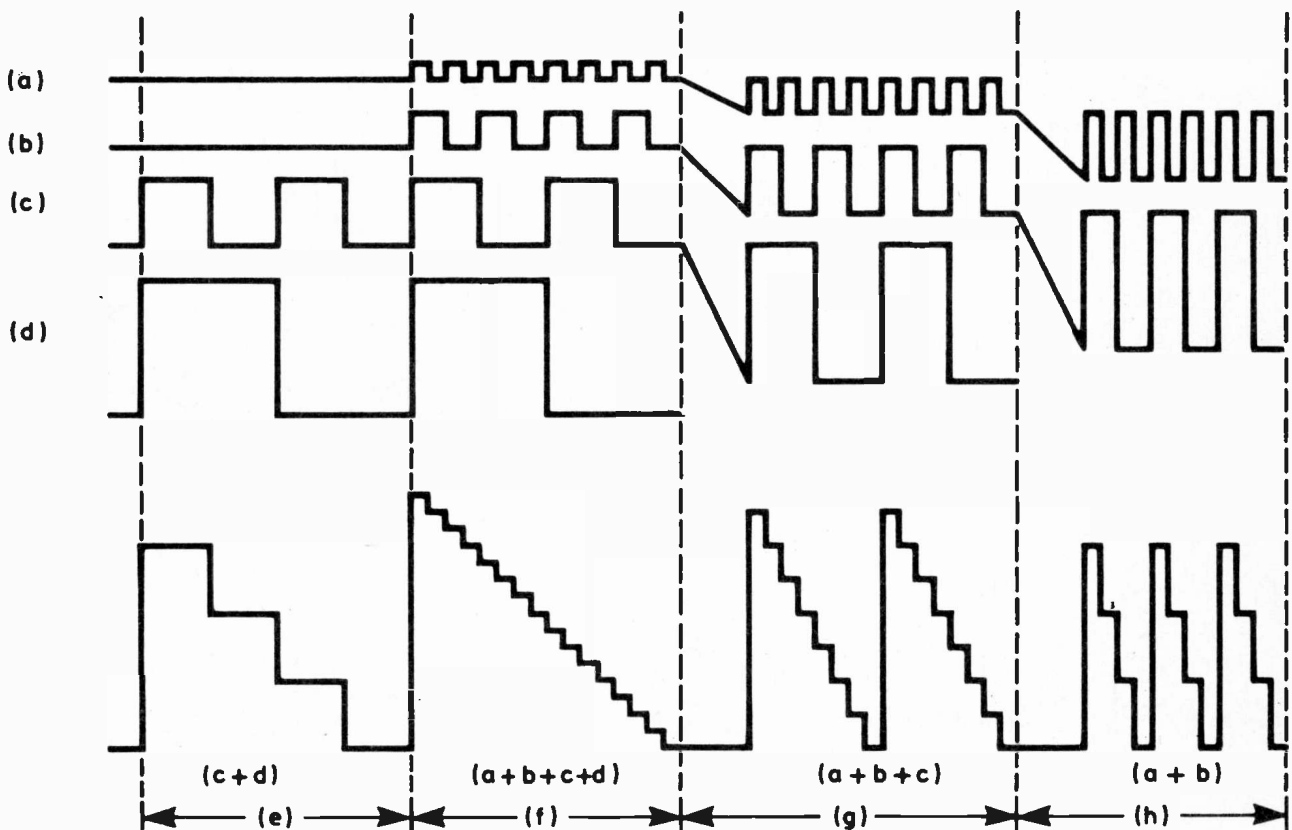


Fig. 4.2. Formation of staircase waveforms from octave related squarewaves

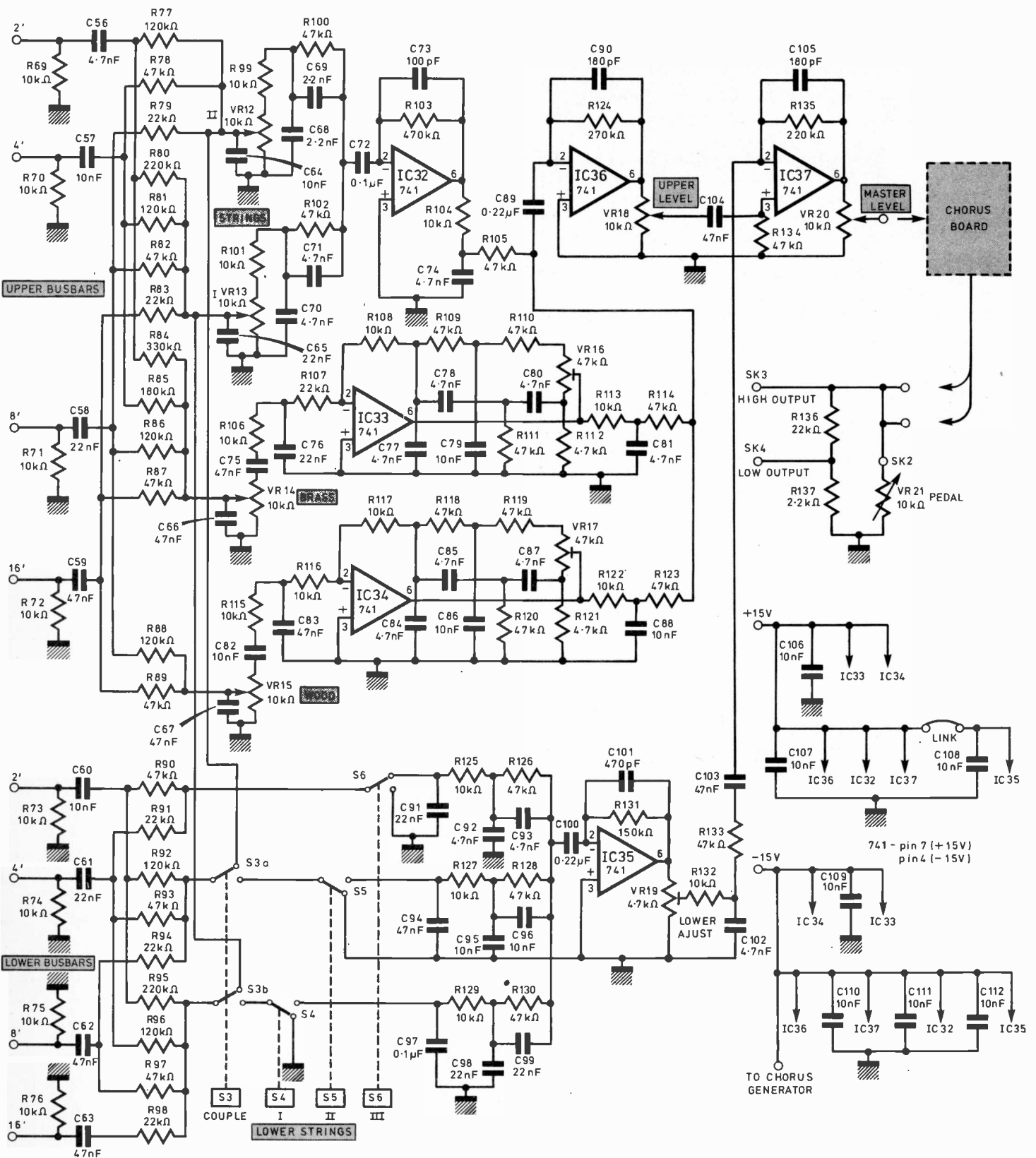


Fig. 4.3. The complete voice circuitry

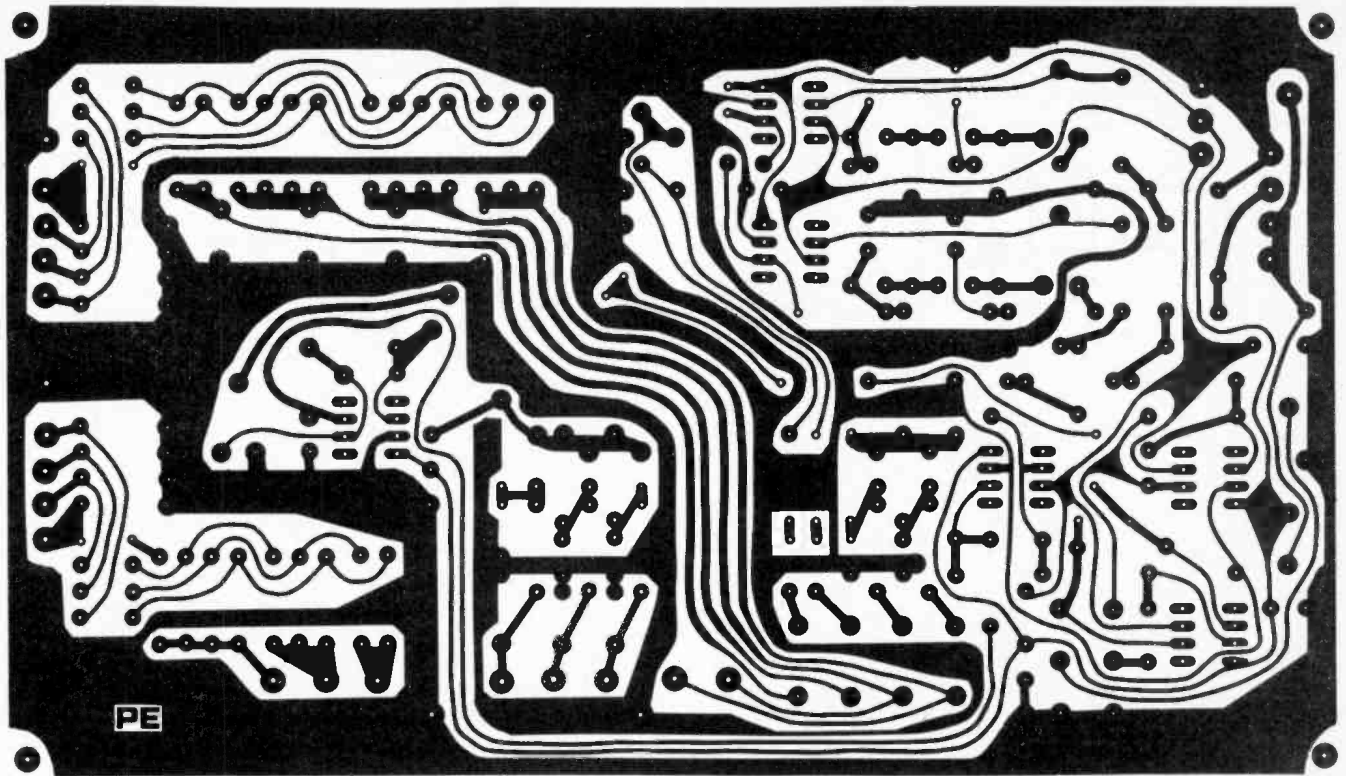


Fig. 4.4. Etching detail for the voice p.c.b.

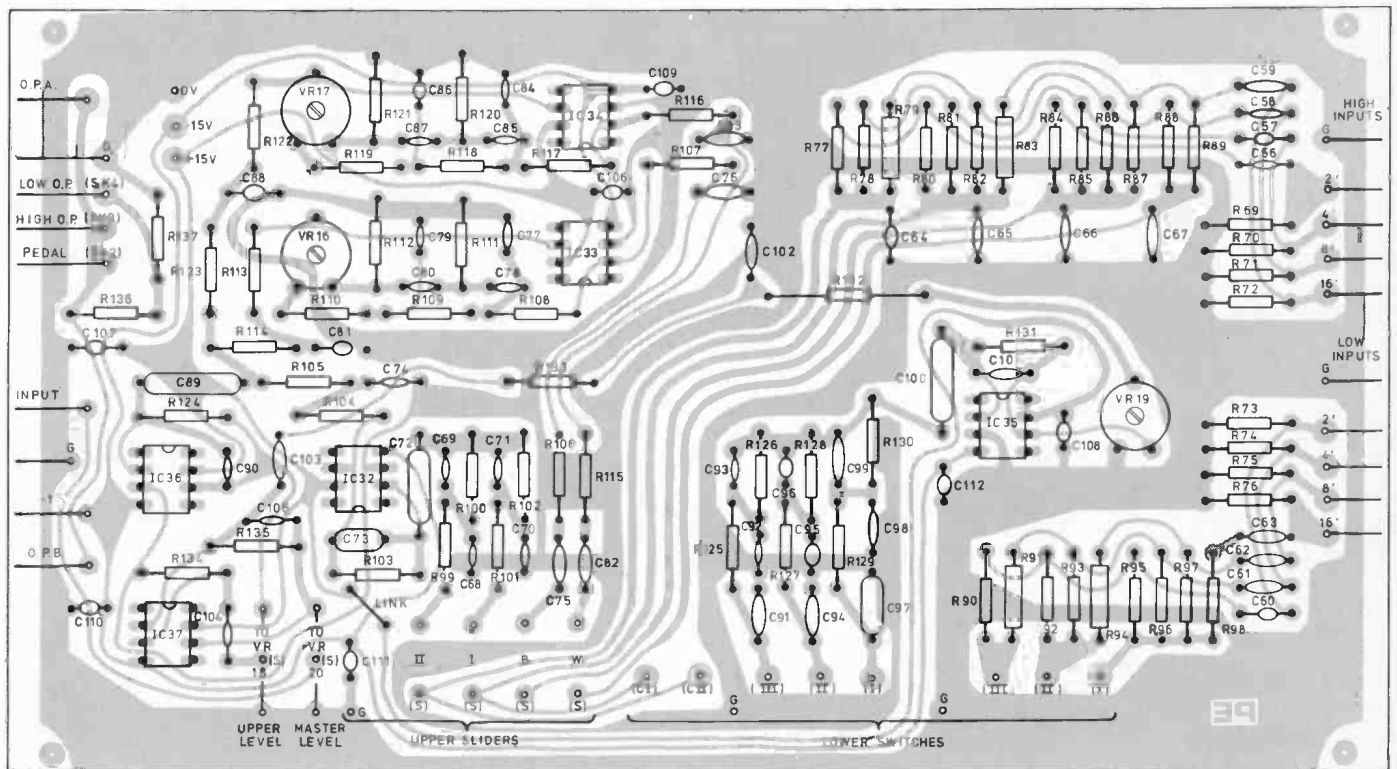


Fig. 4.5. Showing component assembly and drillings

COMPONENTS . . .

VOICING SYSTEM

Resistors

R69-76	10k Ω	R105	47k Ω
R77	120k Ω	R106	10k Ω
R78	47k Ω	R107	22k Ω
R79	22k Ω	R108	10k Ω
R80	220k Ω	R109-111	47k Ω
R81	120k Ω	R112	4.7k Ω
R82	47k Ω	R113	10k Ω
R83	22k Ω	R114	47k Ω
R84	330k Ω	R115-116	10k Ω
R85	180k Ω	R117	10k Ω
R86	120k Ω	R118-120	47k Ω
R87	47k Ω	R121	4.7k Ω
R88	120k Ω	R122	10k Ω
R89-90	47k Ω	R123	47k Ω
R91	22k Ω	R124	270k Ω
R92	120k Ω	R125	10k Ω
R93	47k Ω	R126	47k Ω
R94	22k Ω	R127	10k Ω
R95	220k Ω	R128	47k Ω
R96	120k Ω	R129	10k Ω
R97	47k Ω	R130	47k Ω
R98	22k Ω	R131	150k Ω
R99	10k Ω	R132	10k Ω
R100	47k Ω	R133	47k Ω
R101	10k Ω	R134	47k Ω
R102	47k Ω	R135	220k Ω
R103	470k Ω	R136	22k Ω
R104	10k Ω	R137	2.2k Ω

$\frac{1}{4}$ watt 5% carbon film

Capacitors

C56	4.7nF ceramic	C82	47nF ceramic
C57	10nF ceramic	C83	47nF ceramic
C58	22nF ceramic	C84-85	4.7nF ceramic
C59	47nF ceramic	C86	10nF ceramic
C60	10nF ceramic	C87	4.7nF ceramic
C61	22nF ceramic	C88	10nF ceramic
C62-63	47nF ceramic	C89	0.22 μ F polyester
C64	10nF ceramic	C90	180pF
C65	22nF ceramic	C91	22nF ceramic
C66-67	47nF ceramic	C92-93	4.7nF ceramic
C68-69	2.2nF ceramic	C94	47nF ceramic
C70-71	4.7nF ceramic	C95-96	10nF ceramic
C72	0.1 μ F polyester	C97	0.1 μ F polyester
C73	100pF	C98-99	22nF ceramic
C74	4.7nF ceramic	C100	0.22 μ F polyester
C75	47nF ceramic	C101	470pF ceramic
C76	22nF ceramic	C102	4.7nF ceramic
C77-78	4.7nF ceramic	C103	47nF ceramic
C79	10nF ceramic	C104	47nF ceramic
C80	4.7nF ceramic	C105	180pF
C81	10nF ceramic	C106-112	10nF ceramic

Potentiometers

VR12-15 10k Ω lin Sliders, VR16-17 47k Ω Presets
100mW submin. VR18 10k Ω lin, VR19 4.7k Ω Preset,
VR20 10k Ω lin, VR21 10k Ω Pedal

Integrated Circuits

IC32-37 741

Miscellaneous

SK2-4 Mono standard jack. S3-6 bank of two-pole
two-way switches interlocked. 47 terminal pins
1 printed circuit board.

the 4ft signal is inoperative. S4, 5 and 6 convert the lower section to 16ft, 8ft and 4ft strings only, but more than one control button may be depressed at the same time. Except when in the couple condition the Lower Voices have a fixed amplitude preset by VR19, and balancing of the two parts of the keyboard is achieved with the Upper Level Control.


PREAMPLIFIER

Upper and Lower Voices are fed to the complementary (anti-phase) inputs of preamplifier IC37 to compensate for the additional inverting amplifier, IC36, in the upper voice channel. The main purpose of the Master Level Control VR20 is to compensate for the many modes and styles in which the instrument may be played, either melodic or chordal, single or multi-voiced, and it may be used to prevent overloading of the Chorus Generator input under extreme conditions.

OUTPUT AND SUPPLIES

After processing by the Chorus Generator the signal is returned to the Voice Board on which it is controlled by the Expression Pedal via socket SK2. Divider resistors R136 and R137 give high and low level outputs at SK3 and SK4.

The Voice Board is powered by +15 volt and -15 volt supplies obtained from the regulators on the PSU/Tone Generator Board, and capacitors C106 to C112 are incorporated to ensure stable operation to the 741 Operational Amplifiers.

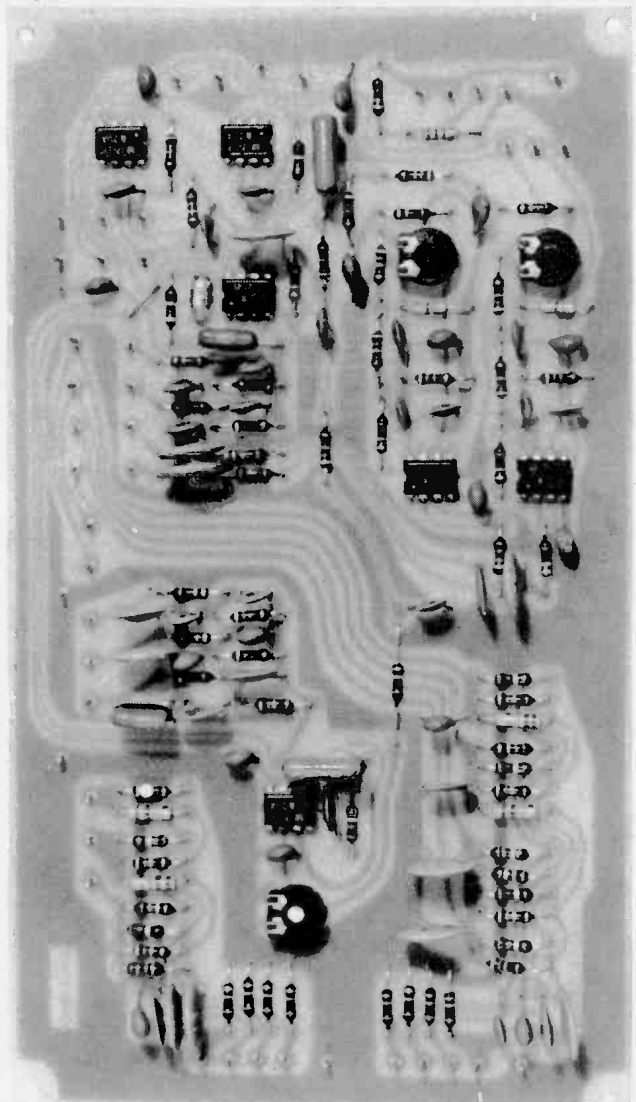

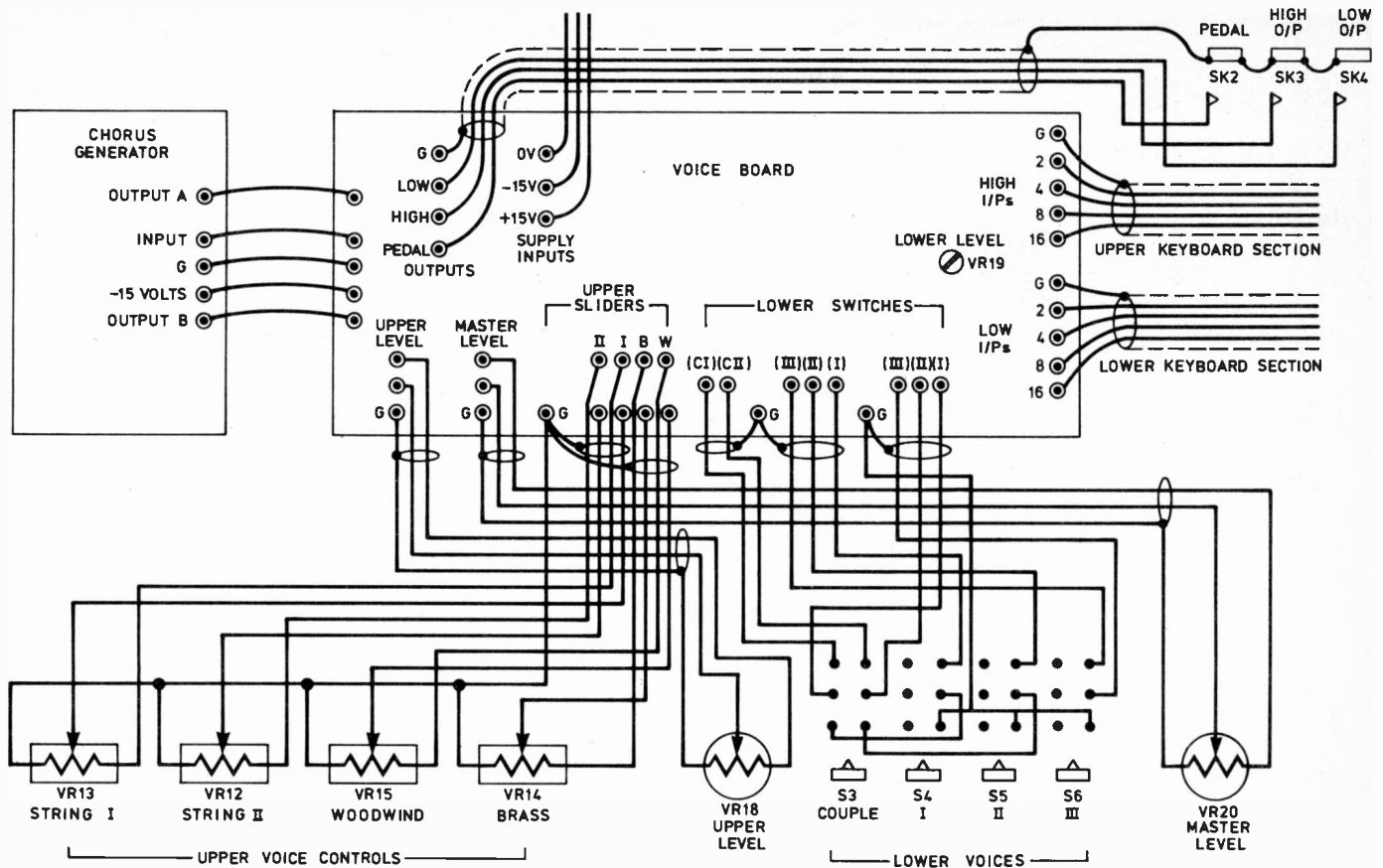


Fig. 4.6. Voice and Chorus interwiring

VOICE BOARD CONSTRUCTION

The Voice circuits described are mounted on a printed circuit board, the etching and drilling details of which are given in Fig. 4.4, with the component assembly details in Fig. 4.5. To assemble the board the terminal pins should first be inserted followed by resistors, i.e.s, preset potentiometers, small capacitors, large capacitors and the wire link next to R103.

INTERWIRING OF THE VOICE AND CHORUS CIRCUITRY

The Chorus Generator interfaces with the Voice Board only, as shown in Fig. 4.6, whilst the Voice Board provides connections to all controls and output sockets. The wiring details given in Fig. 4.6 should be followed carefully, and it should be particularly noted that in some cases screen connections are made at one end of a cable only whilst in others both ends of the screen are connected.

Supply inputs to the Voice Board are taken direct from the PSU/Tone Generator at +15 volts, -15 volts, and 0 volts. Pedal and output signals are taken through a single 3-core screened cable to sockets SK2-SK4 with both ends of the screen connected.

High and low inputs are each taken from the diode gate busbars through a four-core screened cable with the screen connected at each end. The Upper and Master Level Controls are connected by two-core screened cables with the screen soldered at both ends.

UPPER VOICE CONTROLS

A ground lead is taken from the Voice Board and connected to one of the slider controls. A lead is then taken from this point to each voice control potentiometer. The remaining terminals on VR12 and VR13 are connected via a four-core screened cable with the screen soldered at the Voice Board end, but not to the potentiometers. Similarly VR14 and VR15 are connected via a four-core screened cable.

LOWER VOICE SWITCHES

A ground lead is taken to the tags (or pins) shown on S4, S5 and S6, which are strapped together. Three multi-screened leads are then used to complete interconnection to the switches and in each case the screen is only soldered to the Voice Board end whilst the other end is cropped and cleaned up to prevent shorting to other switch connections.

The first lead is two-core and interconnects the relevant pins on the Voice Board to S3. The second lead is three-core and interconnects the Voice Board to S3. The second lead is also three-core and interconnects to the two tags shown on S3 and one tag on S6. Ordinary wire connections are then made as shown between S3 and S4, and between S3 and S5.

Note: Omissions from Part One Components List are C6, C7, C9, C12-10nF ceramic, C8-68pF.

In Fig. 2.5 diodes D23-30 should be reversed. Fig. 2.2 shows them correctly polarised.

In Fig. 3.6 IC28 should be a 14 pin device. The two extreme left pin connections should be ignored.

NEXT MONTH—Cabinet construction